

LIGHT UP AN LED

SCRATCH


Jumper wire

resistor

led


breadboard

GPIO pins

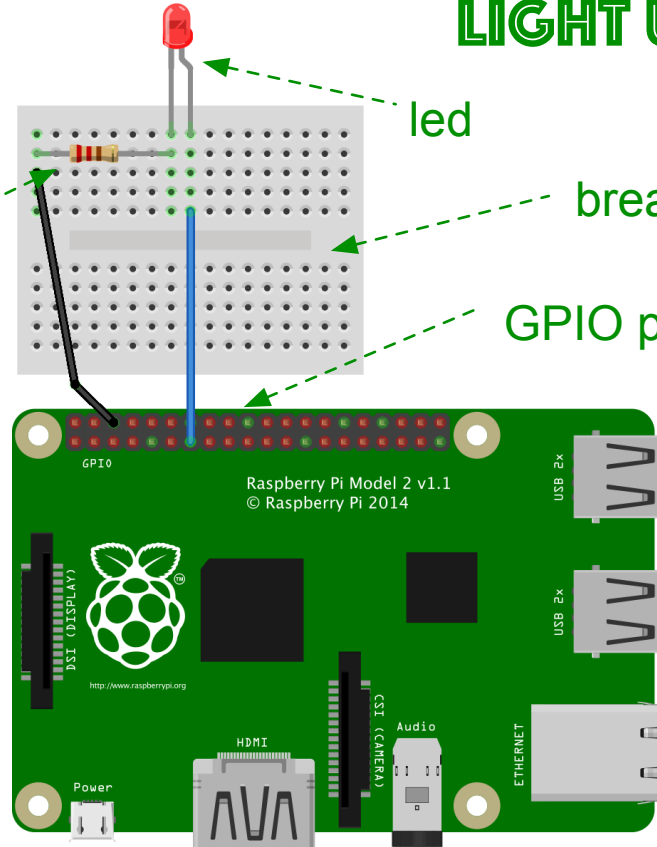

fritzing



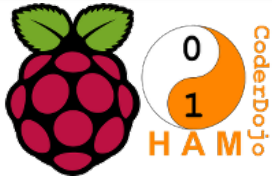

How do you think you can turn the led off?

Can you make the led flash on and off?

