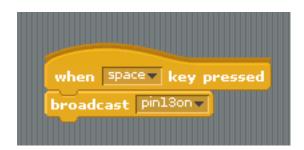
LIGHT UP AN LED led resistor breadboard Jumper wire **GPIO** pins fritzing





How do you think you can turn the led off?

Can you make the led flash on and off?

